
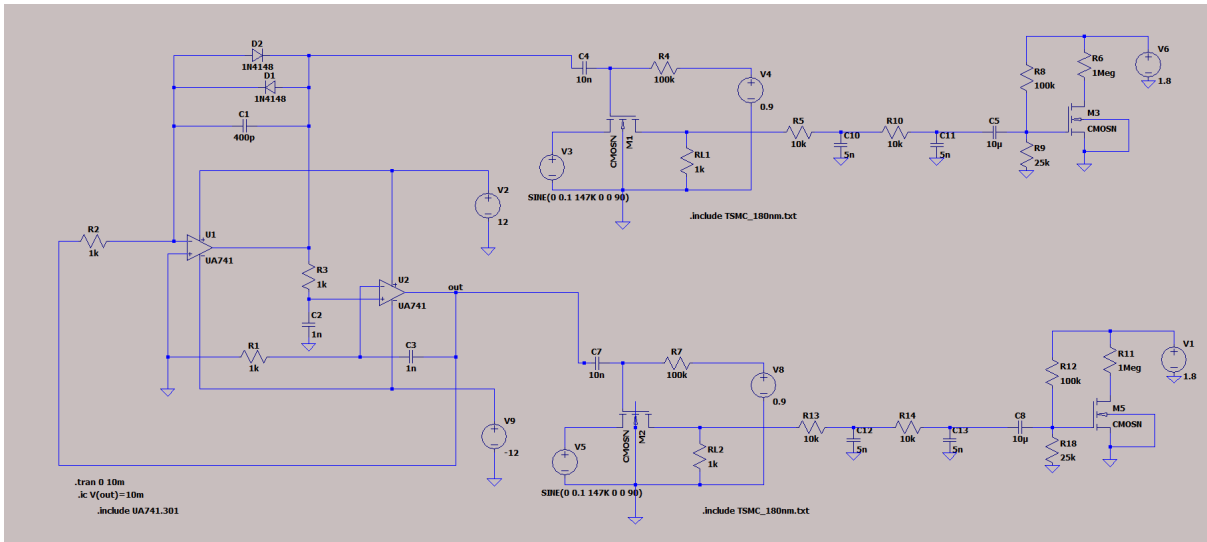


LT Spice Simulation - QDC



Circuit Diagram

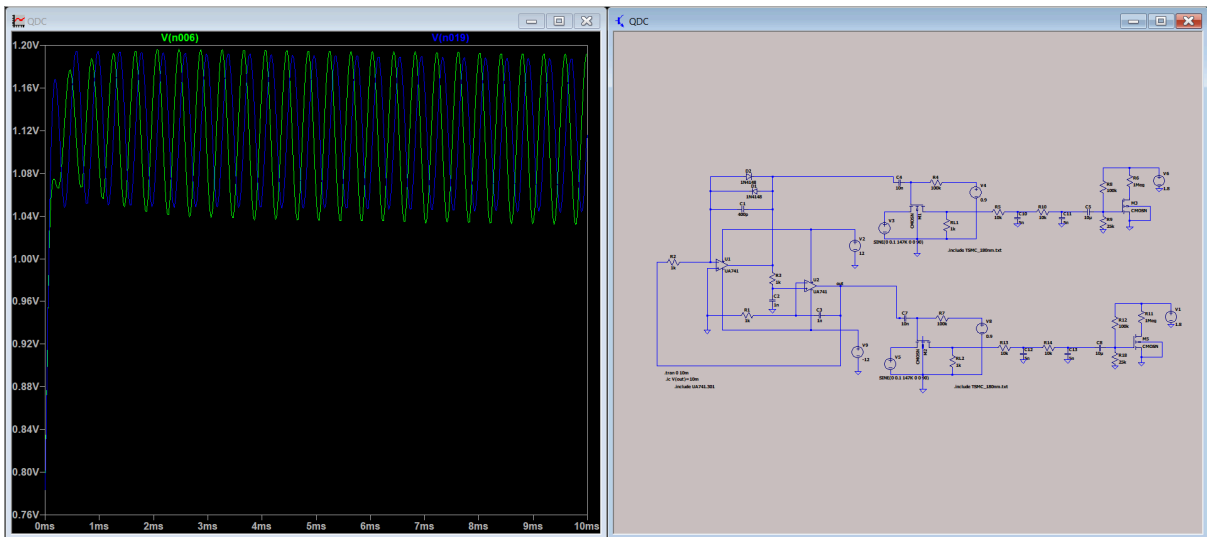



Output





Quadrature Oscillator Output

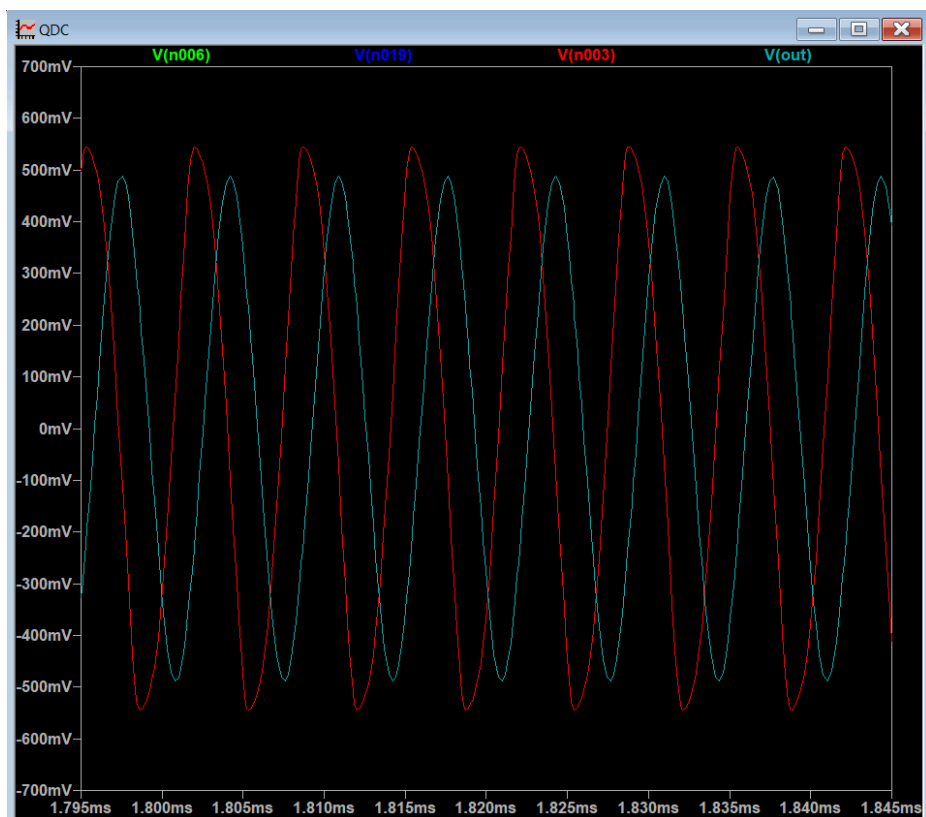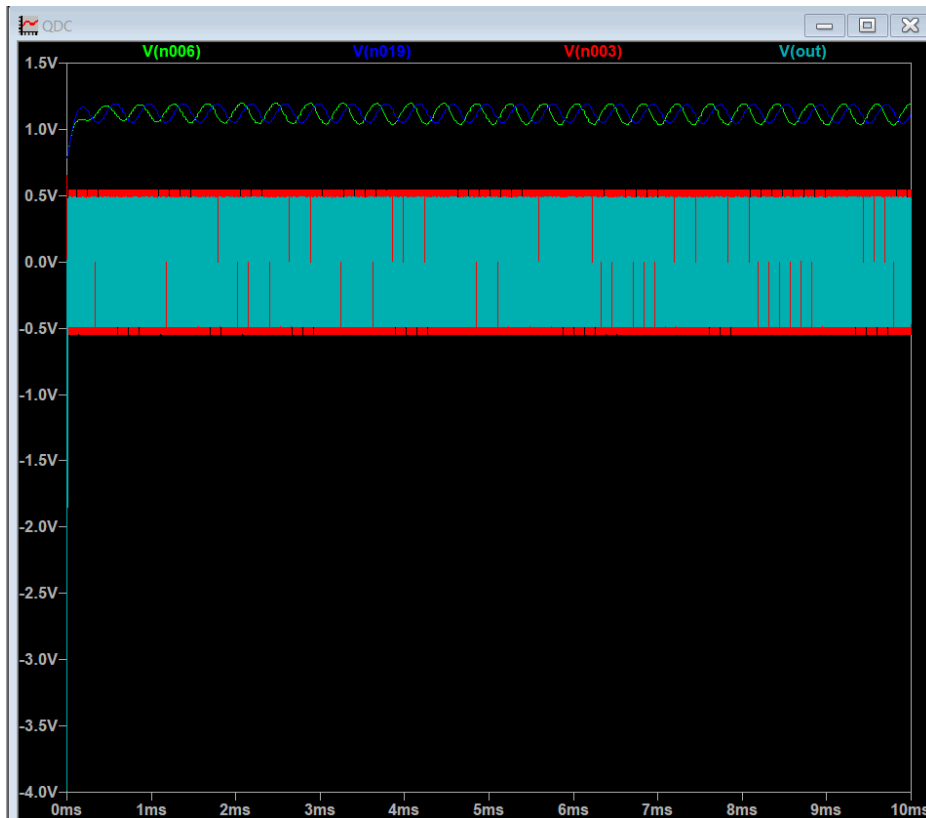

Mixer Output

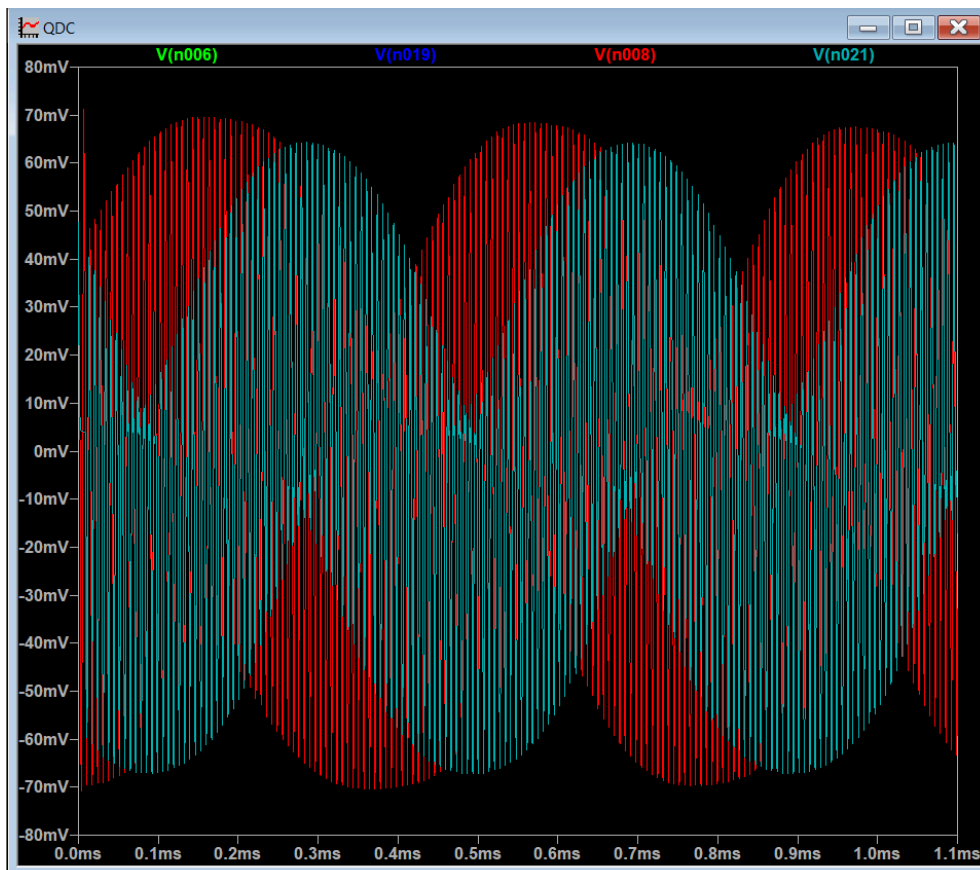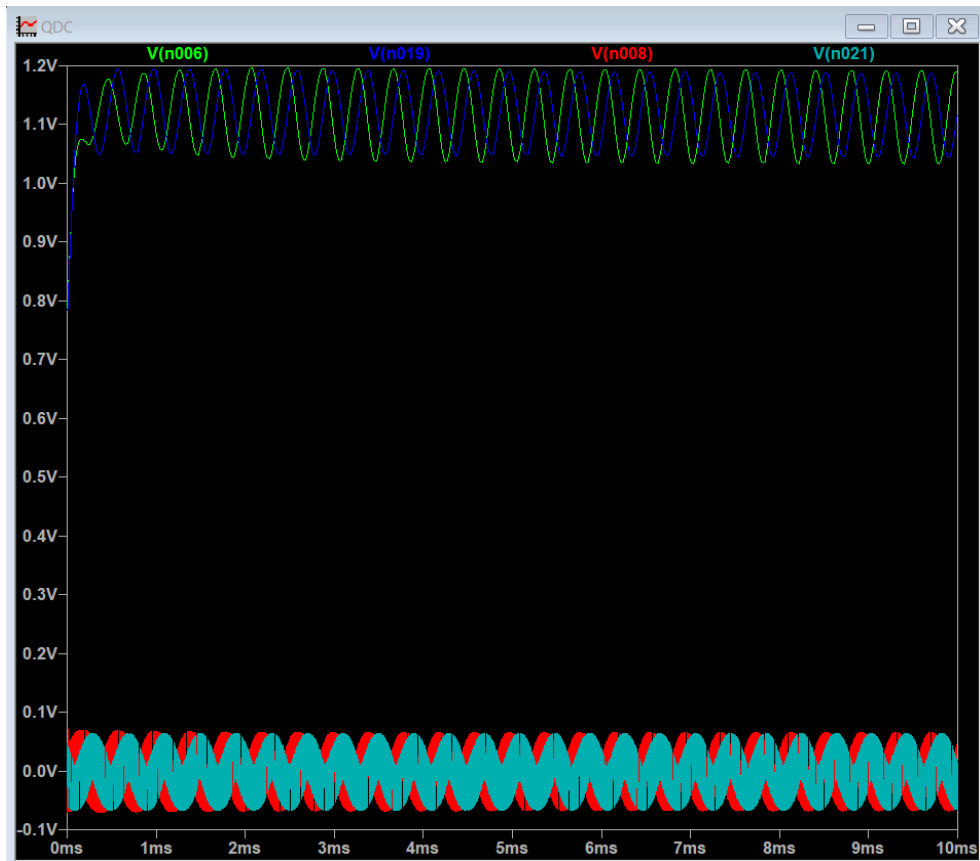

Low Pass Filter Output

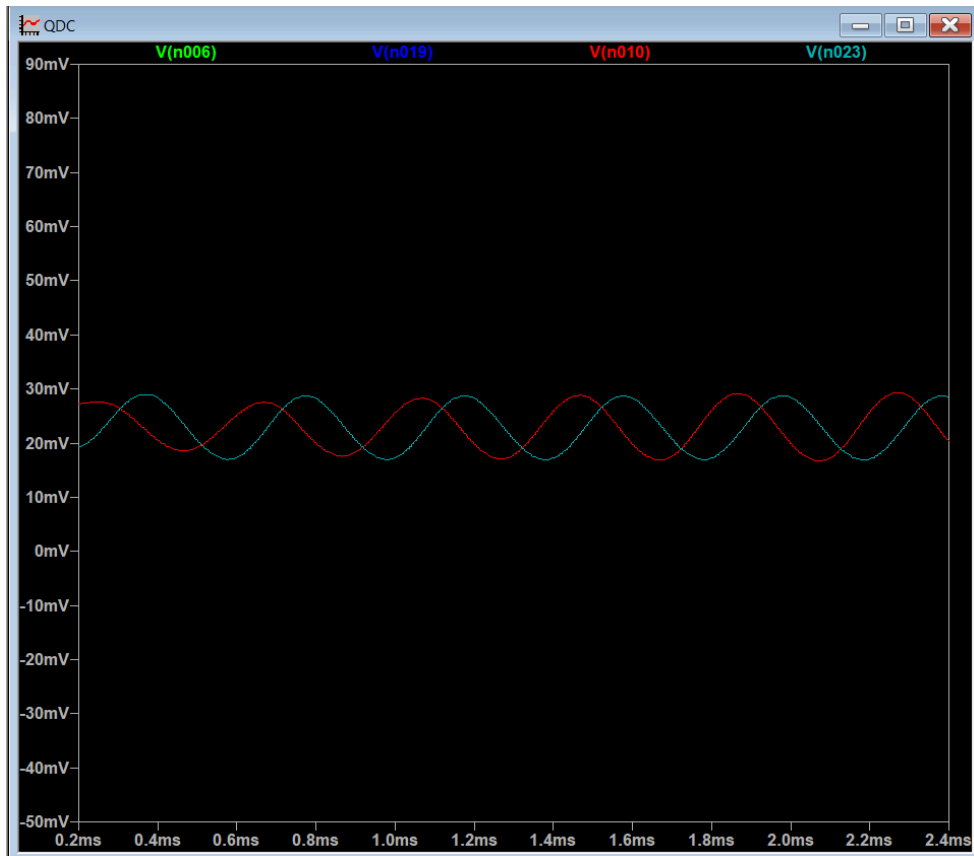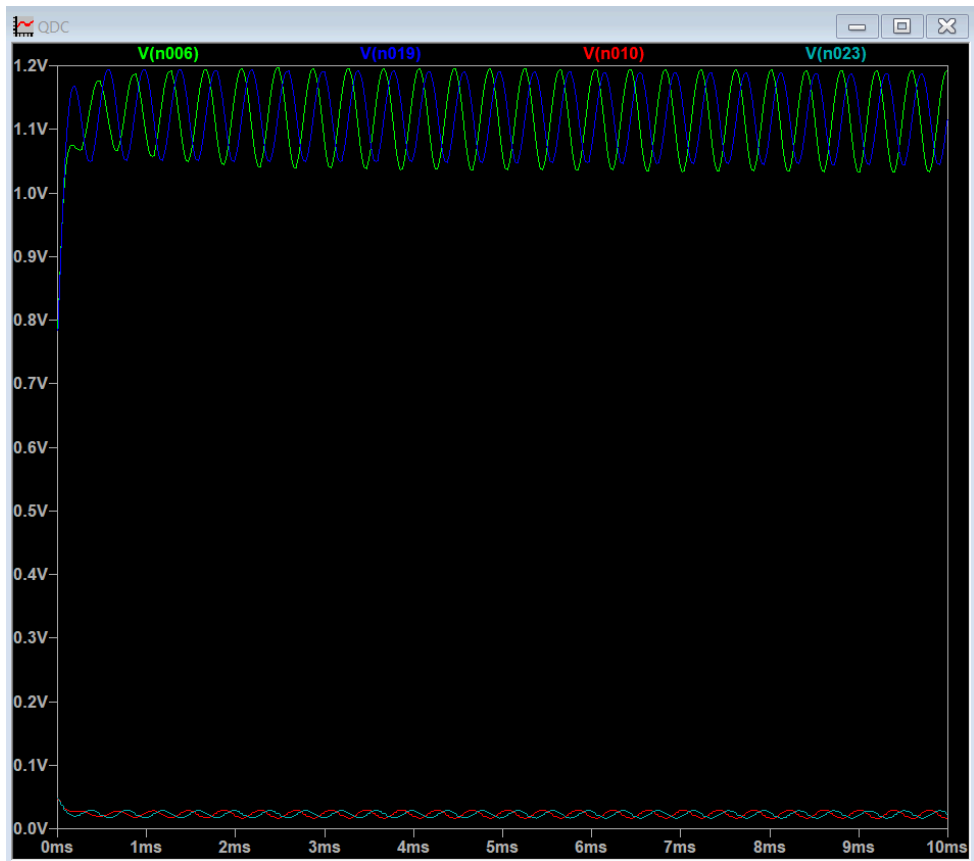

Amplifier Output/Final Output

